

Lab 2

Shahed Ahmed

3/19/2023

CDA3203 Computer Logic Design


Spring 2023

Dr. Maria Petrie

Florida Atlantic University

Part 1: A 1-bit Half Adder to add 2 binary bits (A, B) and results in a 1-bit Sum and 1-bit Carry-out (Cout) with only NAND gates.

Project Settings Snip

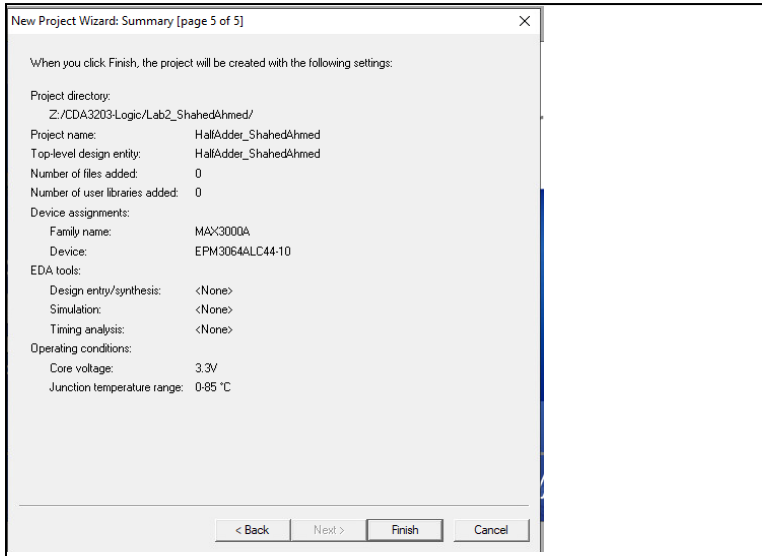


Truth Table


Output
 $A+B$

INPUTS		Count	Sum
A	B	Count	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

K-maps and Simplest Sum of Products

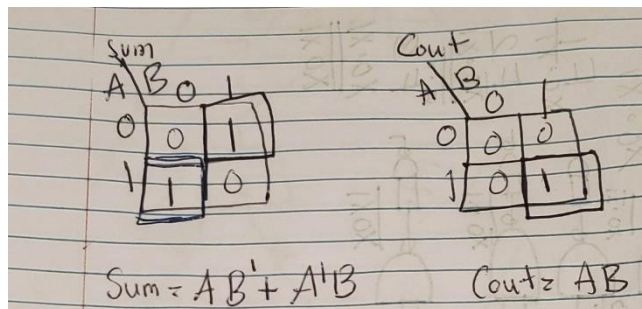

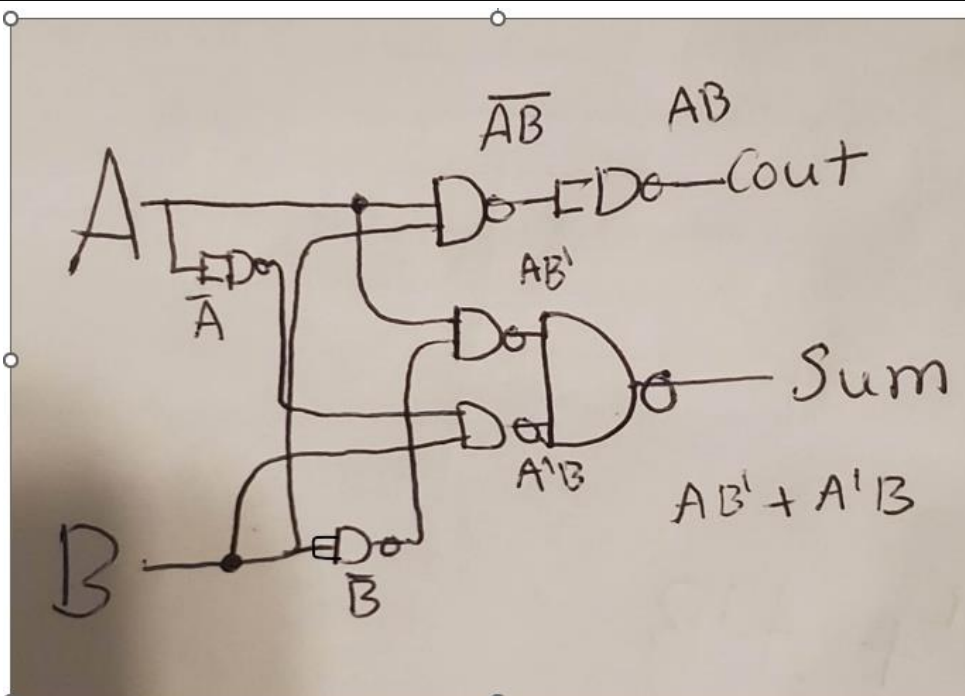Drawing Simplest NAND Circuit equivalent the Simplest Sum of Products



VHDL Code

```
HalfAdder_ShahedAhmed.vhd Simulator Tool

1  -- ShahedAhmed
2  -- DR. Petrie
3  -- HalfAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6  entity HalfAdder_ShahedAhmed is
7
8
9
10
11  port
12  (
13      -- Input ports
14      A,B : in  STD_LOGIC;
15
16      -- Output ports
17      Cout,Sum: out STD_LOGIC
18  );
19  end HalfAdder_ShahedAhmed;
20
21  architecture Structure of HalfAdder_ShahedAhmed is
22
23  begin
24      -- Cout AB
25      Cout <= (A NAND B) NAND (A NAND B);
26      -- Sum AB'+A'B
27      Sum <= ((A NAND A) NAND B) NAND (A NAND (B NAND B));
28  end Structure;
29
```

Successful Compilation

HalfAdder_ShahedAhmed.vhd Simulator Tool

Compiler Tool

Analysis & Synthesis: 100% 00:00:03
Filter: 100% 00:00:01
Assembler: 100% 00:00:02
Classic Timing Analyzer: 100% 00:00:01

Full Compilation: 100% 00:00:07

Start Stop Report

Quartus II


Full Compilation was successful (1 warning)

OK

```
hahedAhmed.vhd


1  -- ShahedAhmed
2  -- DR. Petrie
3  -- HalfAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6  entity HalfAdder_ShahedAhmed is
7
8
9
10
11  port
12  (
13      -- Input ports
14      A,B : in  STD_LOGIC;
15
16      -- Output ports
17      Cout,Sum: out STD_LOGIC
18  );
19  end HalfAdder_ShahedAhmed;
20
21  architecture Structure of HalfAdder_ShahedAhmed is
22
23  begin
24      -- Cout AB
25      Cout <= (A NAND B) NAND (A NAND B);
26      -- Sum AB'+A'B
27      Sum <= ((A NAND A) NAND B) NAND (A NAND (B NAND B));
28  end Structure;
29
```

Timing Diagram

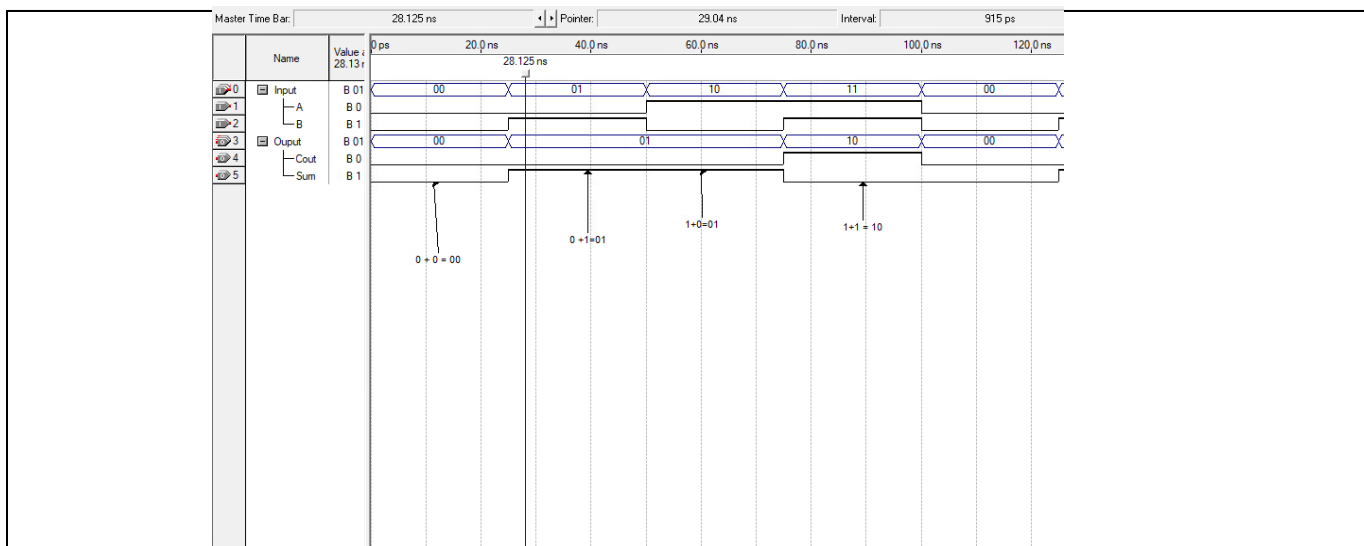

Part 2: A 1-bit Full Adder to add 2 binary bits (A, B) and a 1-bit Carry-in (Cin) and results in a 1-bit Sum and 1-bit Carry-out (Cout) with only NAND gates.


Project Settings Snip

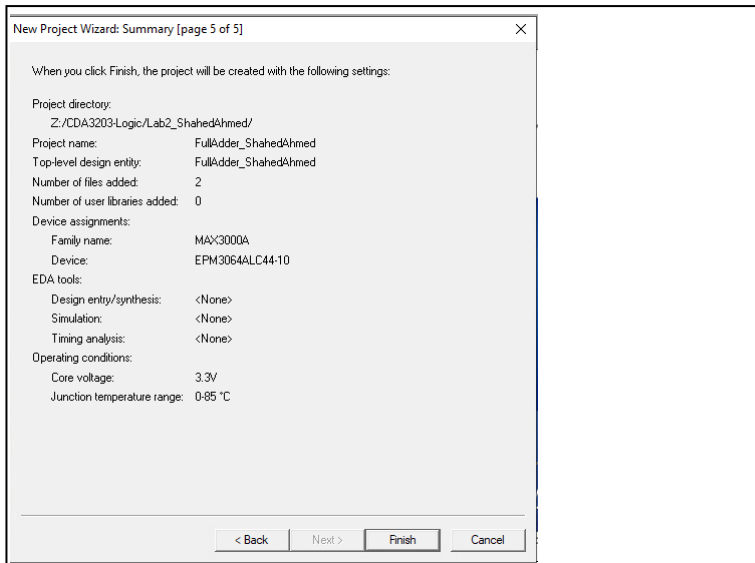


Truth Table

A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

K-maps and Simplest Sum of Products

 

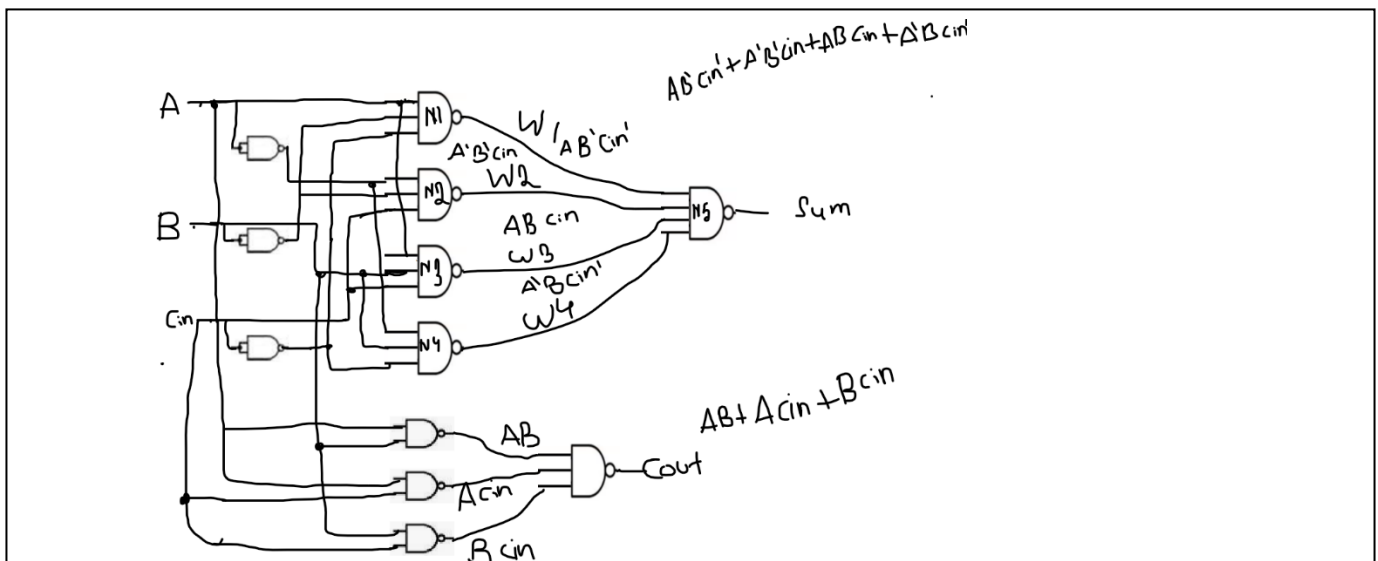Drawing Simplest NAND Circuit equivalent the Simplest Sum of Products



VHDL Code

```
FullAdder_ShahedAhmed.vhd Simulator Tool
1  -- ShahedAhmed -- DR.petrie -- FullAdder With NAND3 and NAAND 4
2  library ieee;
3  use ieee.std_logic_1164.all;
4  entity FullAdder_ShahedAhmed is
5
6      port
7      (
8          -- Input ports
9          A,B,Cin : in STD_LOGIC;
10         -- Output ports
11         Cout,Sum: out STD_LOGIC
12     );
13 end FullAdder_ShahedAhmed;
14
15 architecture Structure of FullAdder_ShahedAhmed is
16     SIGNAL W1,W2,W3,W4 : STD_LOGIC;
17
18     COMPONENT NAND3_ShahedAhmed is
19     port
20     (
21         A,B,C : in STD_LOGIC;
22         x      : out STD_LOGIC;
23     );
24 end COMPONENT NAND3_ShahedAhmed;
25
26     COMPONENT NAND4_ShahedAhmed is
27     port
28     (
29         A,B,C,D : in STD_LOGIC;
30         x        : out STD_LOGIC;
31     );
32 end COMPONENT NAND4_ShahedAhmed;
33
34 begin
35     --- sum
36     N1: NAND3_ShahedAhmed PORT MAP (A, (B NAND B), (Cin NAND Cin),W1);
37     N2: NAND3_ShahedAhmed PORT MAP ((A NAND A), (B NAND B), Cin,W2);
38     N3: NAND3_ShahedAhmed PORT MAP (A,B,Cin,W3);
39     N4: NAND3_ShahedAhmed PORT MAP ((A NAND A),B, (Cin NAND Cin),W4);
40     N5: NAND4_ShahedAhmed PORT MAP (W1,W2,W3,W4,Sum);
41
42     --- cout
43     C1:NAND3_ShahedAhmed PORT MAP (A NAND B,A NAND Cin,B NAND Cin,Cout);
44 end Structure;
```

Successful Compilation

FullAdder_ShahedAhmed.vhd Compiler Tool

FullAdder_ShahedAhmed.vhd

```
1  -- ShahedAhmed -- DR.petrie -- FullAdder With NAND3 and NAAND 4
2  library ieee;
3  use ieee.std_logic_1164.all;
4  entity FullAdder_ShahedAhmed is
5
6      port
7      (
8          -- Input ports
9          A,B,Cin : in STD_LOGIC;
10         -- Output ports
11         Cout,Sum: out STD_LOGIC
12     );
13 end FullAdder_ShahedAhmed;
14
15 architecture Structure of FullAdder_ShahedAhmed is
16     SIGNAL W1,W2,W3,W4 : STD_LOGIC;
17
18     COMPONENT NAND3_ShahedAhmed is
19     port
20     (
21         A,B,C : in STD_LOGIC;
22         x      : out STD_LOGIC;
23     );
24 end COMPONENT NAND3_ShahedAhmed;
25
26     COMPONENT NAND4_ShahedAhmed is
27     port
28     (
29         A,B,C,D : in STD_LOGIC;
30         x        : out STD_LOGIC;
31     );
32 end COMPONENT NAND4_ShahedAhmed;
33
34 begin
35     --- sum
36     N1: NAND3_ShahedAhmed PORT MAP (A, (B NAND B), (Cin NAND Cin),W1);
37     N2: NAND3_ShahedAhmed PORT MAP ((A NAND A), (B NAND B), Cin,W2);
38     N3: NAND3_ShahedAhmed PORT MAP (A,B,Cin,W3);
39     N4: NAND3_ShahedAhmed PORT MAP ((A NAND A),B, (Cin NAND Cin),W4);
40     N5: NAND4_ShahedAhmed PORT MAP (W1,W2,W3,W4,Sum);
41
42     --- cout
43     C1:NAND3_ShahedAhmed PORT MAP (A NAND B,A NAND Cin,B NAND Cin,Cout);
44 end Structure;
```

Compiler Tool

Analysis & Synthesis: 100% 00:00:04
Filter: 100% 00:00:02
Assembler: 100% 00:00:02
Classic Timing Analyzer: 100% 00:00:01

Full Compilation: 100% 00:00:09


Start Stop Report

Quartus II

Full Compilation was successful (1 warning)


OK

Timing Diagram

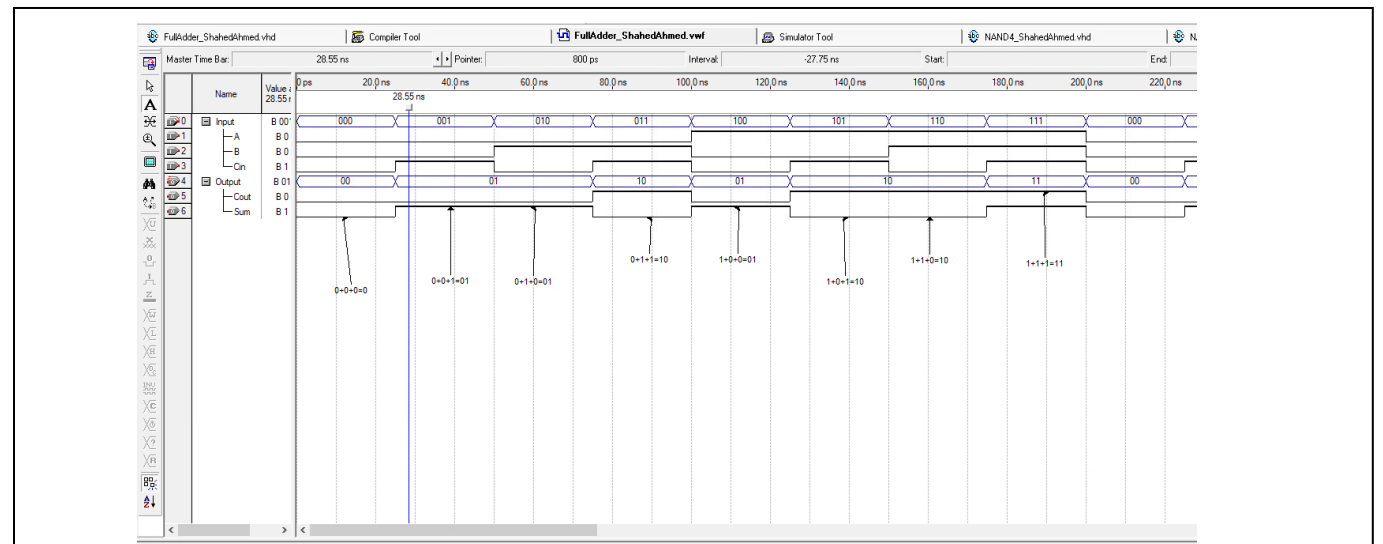


Part 3: A 4-bit Adder to add 2 4 bit binary numbers (A3,A2,A1,A0 and B3,B2,B1,B0 with A0 and B0 being least significant bits) and a 1-bit Carry-in (Cin), and results in a 4-bit Sum (S3,S2,S1,S0) and 1-bit Carry-out (Cout) with the 1-bit Full Adder component you built.

Project Settings Snip

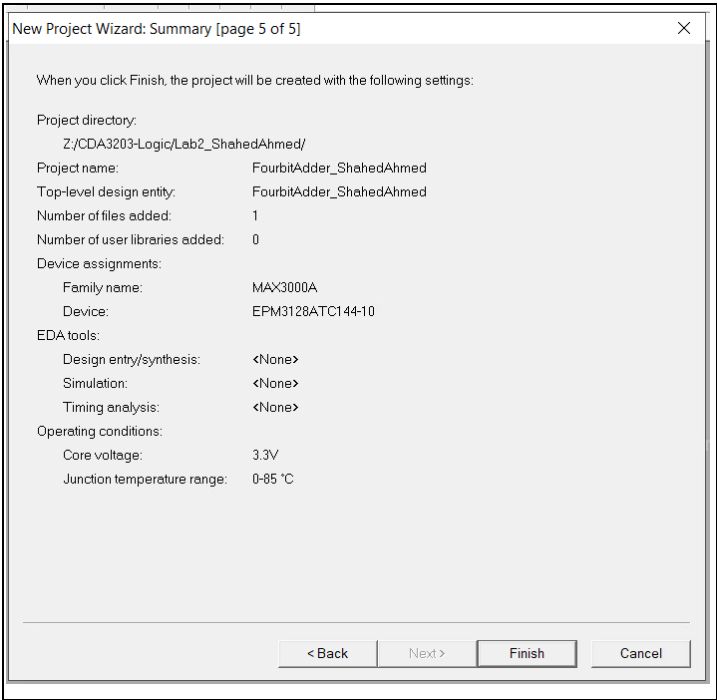

Draw of your circuit

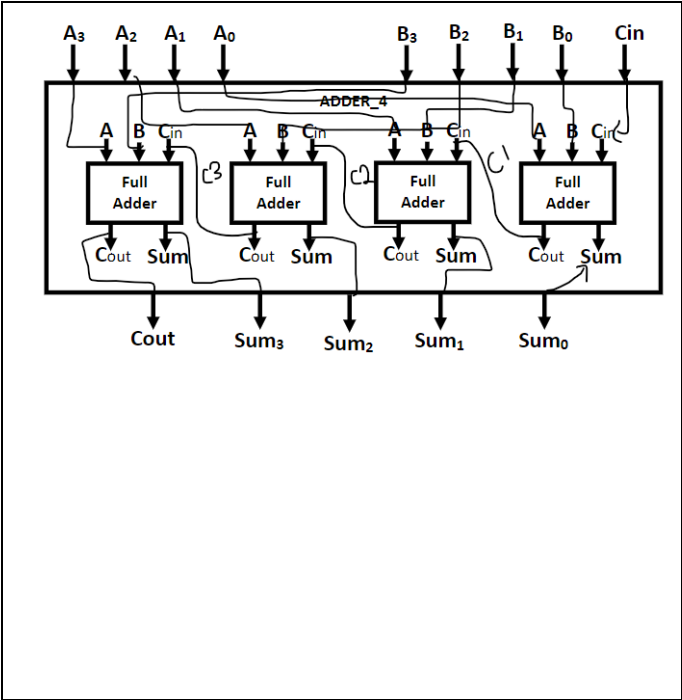

VHDL Code

```

fourbitadder_shahedahmed.vhd
fourbitadder_shahedahmed.vhd
1  -- ShahedAhmed
2  -- Dr.petrie
3  -- 4bit FullAdder with FullAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  use work.add_package_ShahedAhmed.all;
8  entity FourbitAdder_ShahedAhmed is
9
10     port
11     (
12         Cin: in  STD_LOGIC;
13         A,B: in  STD_LOGIC_VECTOR(3 DOWNTO 0);
14         S  : out STD_LOGIC_VECTOR(3 DOWNTO 0);
15         Cout: out STD_LOGIC);
16  end FourbitAdder_ShahedAhmed;
17
18
19  architecture Structure of FourbitAdder_ShahedAhmed is
20
21      SIGNAL C : STD_LOGIC_VECTOR(3 DOWNTO 1);
22
23  begin
24      S0: FullAdder_ShahedAhmed PORT MAP (A(0), B(0), Cin,  C(1), S(0)) ;
25      S1: FullAdder_ShahedAhmed PORT MAP (A(1), B(1), C(1), C(2), S(1)) ;
26      S2: FullAdder_ShahedAhmed PORT MAP (A(2), B(2), C(2), C(3), S(2)) ;
27      S3: FullAdder_ShahedAhmed PORT MAP (A(3), B(3), C(3), Cout, S(3)) ;
28
29
30  end Structure ;


```

Successful Compilation

The screenshot displays the Quartus II IDE with the 'fourbitadder_shahedahmed.vhd' file open. The code defines a 4-bit adder entity with inputs A, B, and Cin, and outputs S and Cout. The architecture uses four instances of a 'FullAdder' component. The 'Compiler Tool' window is open, showing that all compilation steps (Analysis & Synthesis, Filter, Assembler, Classic Timing Analyzer) are 100% complete. A 'Full Compilation' progress bar is also at 100%. A message box titled 'Quartus II' states: 'Full Compilation was successful (4 warnings)'.


```
1  -- ShahedAhmed
2  -- Dr.petrie
3  -- 4bit FullAdder with FullAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  use work.add_package_ShahedAhmed.all;
8  entity FourbitAdder_ShahedAhmed is
9
10
11  port
12  (
13      Cin: in  STD_LOGIC;
14      A,B: in  STD_LOGIC_VECTOR(3 DOWNTO 0);
15      S : out STD_LOGIC_VECTOR(3 DOWNTO 0);
16      Cout: out STD_LOGIC);
17  end FourbitAdder_ShahedAhmed;
18
19  architecture Structure of FourbitAdder_ShahedAhmed is
20
21      SIGNAL C : STD_LOGIC_VECTOR(3 DOWNTO 1);
22
23  begin
24      S0: FullAdder_ShahedAhmed PORT MAP (A(0), B(0), Cin, C(1), S(0)) ;
25      S1: FullAdder_ShahedAhmed PORT MAP (A(1), B(1), C(1), C(2), S(1)) ;
26      S2: FullAdder_ShahedAhmed PORT MAP (A(2), B(2), C(2), C(3), S(2)) ;
27      S3: FullAdder_ShahedAhmed PORT MAP (A(3), B(3), C(3), Cout, S(3)) ;
28
29  end Structure ;
30
31
```

Timing Diagram

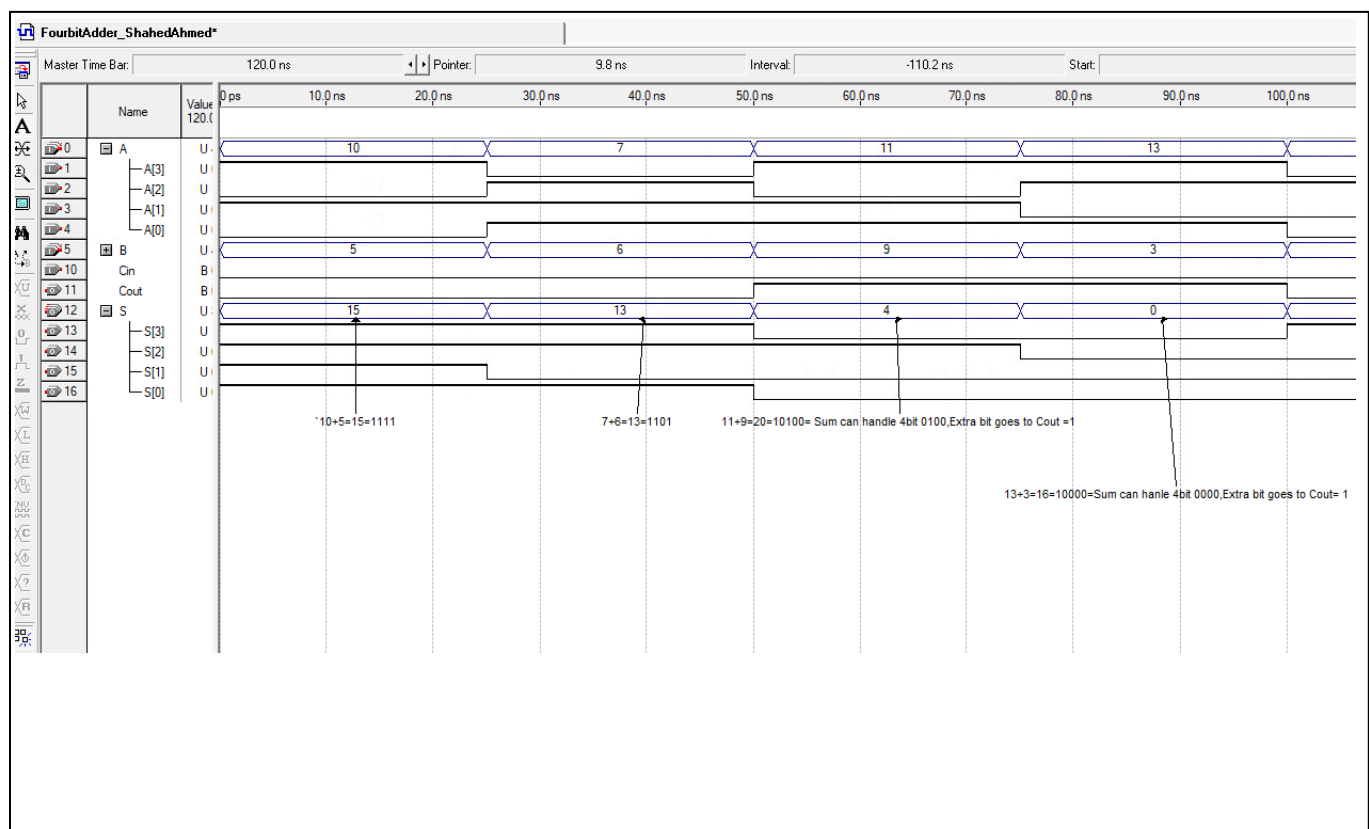


Part 4: A 8-bit Adder to add 2 8-bit binary numbers (A7,A6,A5,A4,A3,A2,A1,A0 and B7,B6,B5,B4,B3,B2,B1,B0 with A0 and B0 being least significant bits) and a 1-bit Carry-in (Cin), and results in a 4-bit Sum (S7,S6,S5,S4,S3,S2,S1,S0) and 1-bit Carry-out (Cout) with the 1-bit Full Adder component you built.

Project Settings Snip

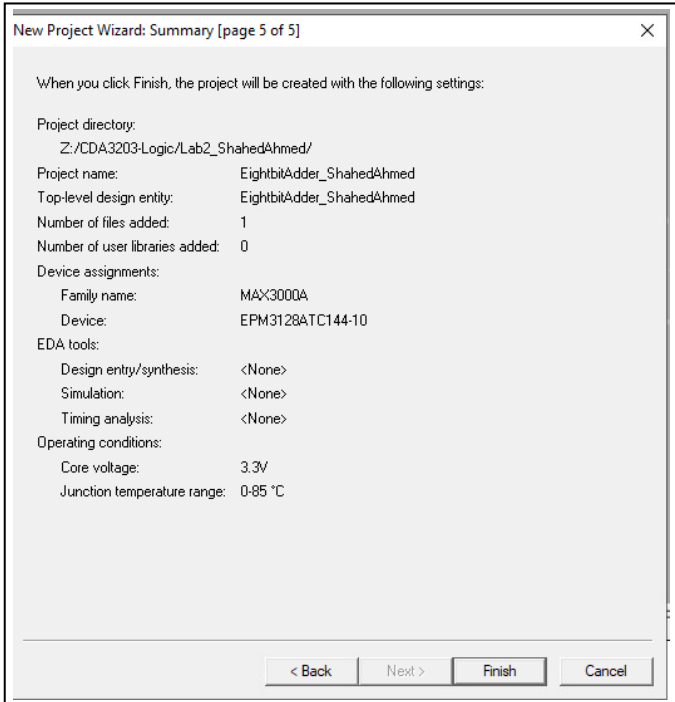

Draw your circuit HERE

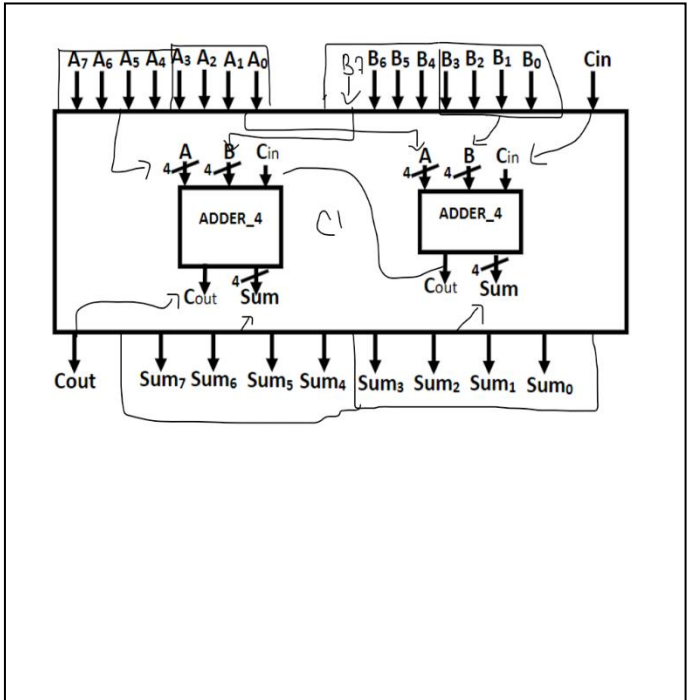

VHDL Code

```

1  --Shahed Ahmed
2  -- Dr.Petrie
3  --8 bitFullAdder With 4bitFullAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use work.add_package_ShahedAhmed.all;
7  entity EightbitAdder_ShahedAhmed is
8
9      Port
10     (
11         Cin: in  STD_LOGIC;
12         A,B: in  STD_LOGIC_VECTOR(7 DOWNTO 0);
13         S  : out STD_LOGIC_VECTOR(7 DOWNTO 0);
14         Cout: out STD_LOGIC);
15 end EightbitAdder_ShahedAhmed;
16
17 architecture Structure of EightbitAdder_ShahedAhmed is
18     SIGNAL C : STD_LOGIC_VECTOR(1 DOWNTO 0);
19 begin
20     S1:FourbitAdder_ShahedAhmed PORT MAP(Cin,A(3 DOWNTO 0),B(3 DOWNTO 0),S(3 DOWNTO 0),C(1));
21     S2:FourbitAdder_ShahedAhmed PORT MAP(C(1),A(7 DOWNTO 4),B(7 DOWNTO 4),S(7 DOWNTO 4),Cout);
22
23 end Structure;
24


```


Successful Compilation

The screenshot displays the Quartus II IDE with the VHDL code for `EightbitAdder_ShahedAhmed.vhd` on the left and the **Compiler Tool** window on the right. The code defines an 8-bit adder entity with inputs `Cin`, `A`, and `B`, and outputs `S` and `Cout`. The `Compiler Tool window shows that all compilation steps (Analysis & Synthesis, Filter, Assembler, and Classic Timing Analyzer) are 100% complete. A Full Compilation progress bar is also at 100%. A message box in the bottom right corner confirms: "Full Compilation was successful (5 warnings)".`


```
1  --Shahed Ahmed
2  -- Dr.Petrie
3  --8 bitFullAdder With 4bitFullAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use work.add_package_ShahedAhmed.all;
7  entity EightbitAdder_ShahedAhmed is
8
9      Port
10     (
11         Cin: in  STD_LOGIC;
12         A,B: in  STD_LOGIC_VECTOR(7 DOWNTO 0);
13         S  : out STD_LOGIC_VECTOR(7 DOWNTO 0);
14         Cout: out STD_LOGIC);
15 end EightbitAdder_ShahedAhmed;
16
17 architecture Structure of EightbitAdder_ShahedAhmed is
18     SIGNAL C : STD_LOGIC_VECTOR(1 DOWNTO 0);
19 begin
20     S1:FourbitAdder_ShahedAhmed PORT MAP (Cin,A(3 DOWNTO 0),B(3 DOWNTO 0),S(3 DOWNTO 0),C(1));
21     S2:FourbitAdder_ShahedAhmed PORT MAP (C(1),A(7 DOWNTO 4),B(7 DOWNTO 4),S(7 DOWNTO 4),Cout);
22
23 end Structure;
```

Timing Diagram

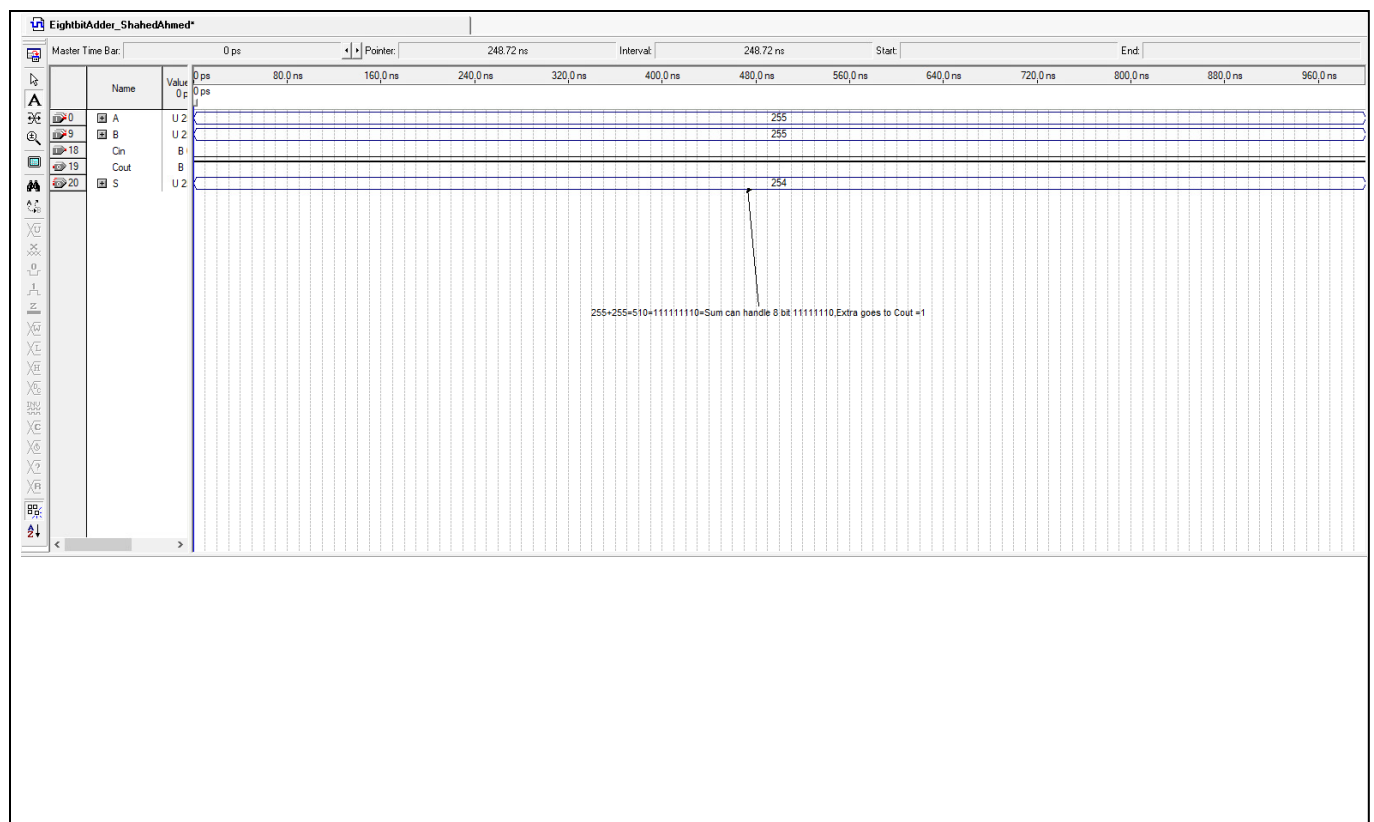


Part 5: A 16-bit Adder to add 2 16-bit binary numbers(A15,A14,A13,A12,A11,A10,A9,A8,A7,A6,A5,A4,A3,A2,A1,A0 and B15,B14,B13,B12,B11,B10,B9,B8,B7,B6,B5,B4,B3,B2,B1,B0 with A0 and B0 being least significant bits) and a 1-bit Carry-in (Cin), and results in a 16-bit Sum (S15,S14,S13,S12,S11,S10,S9,S8,S7,S6,S5,S4,S3,S2,S1,S0) and 1-bit Carry-out (Cout) with component you built


Project Settings Snip

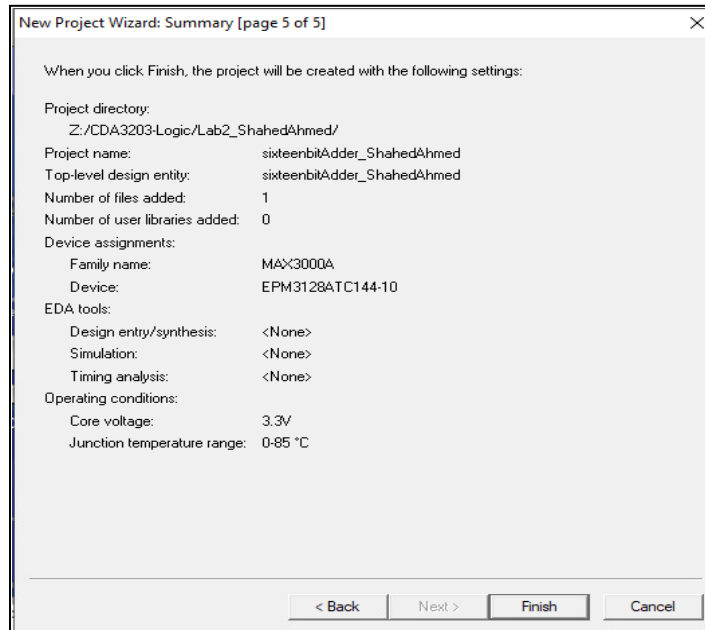

Draw your circuit Here

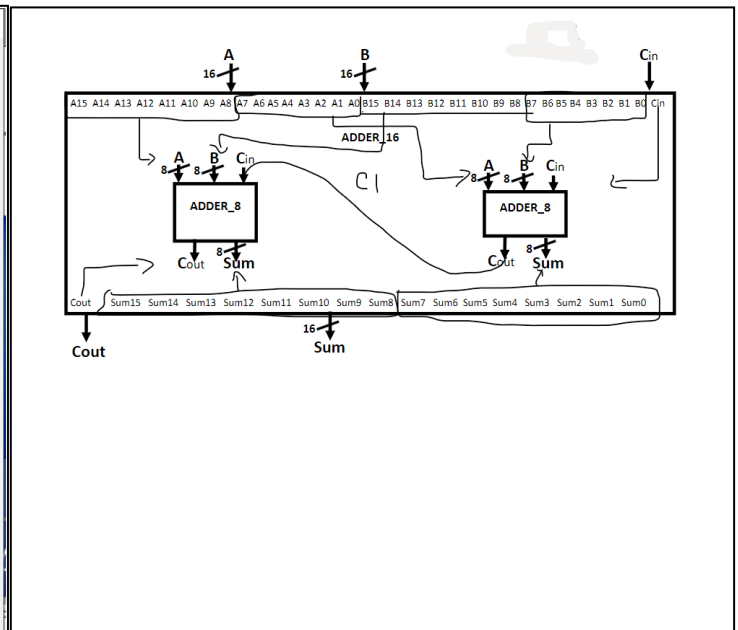

VHDL Code

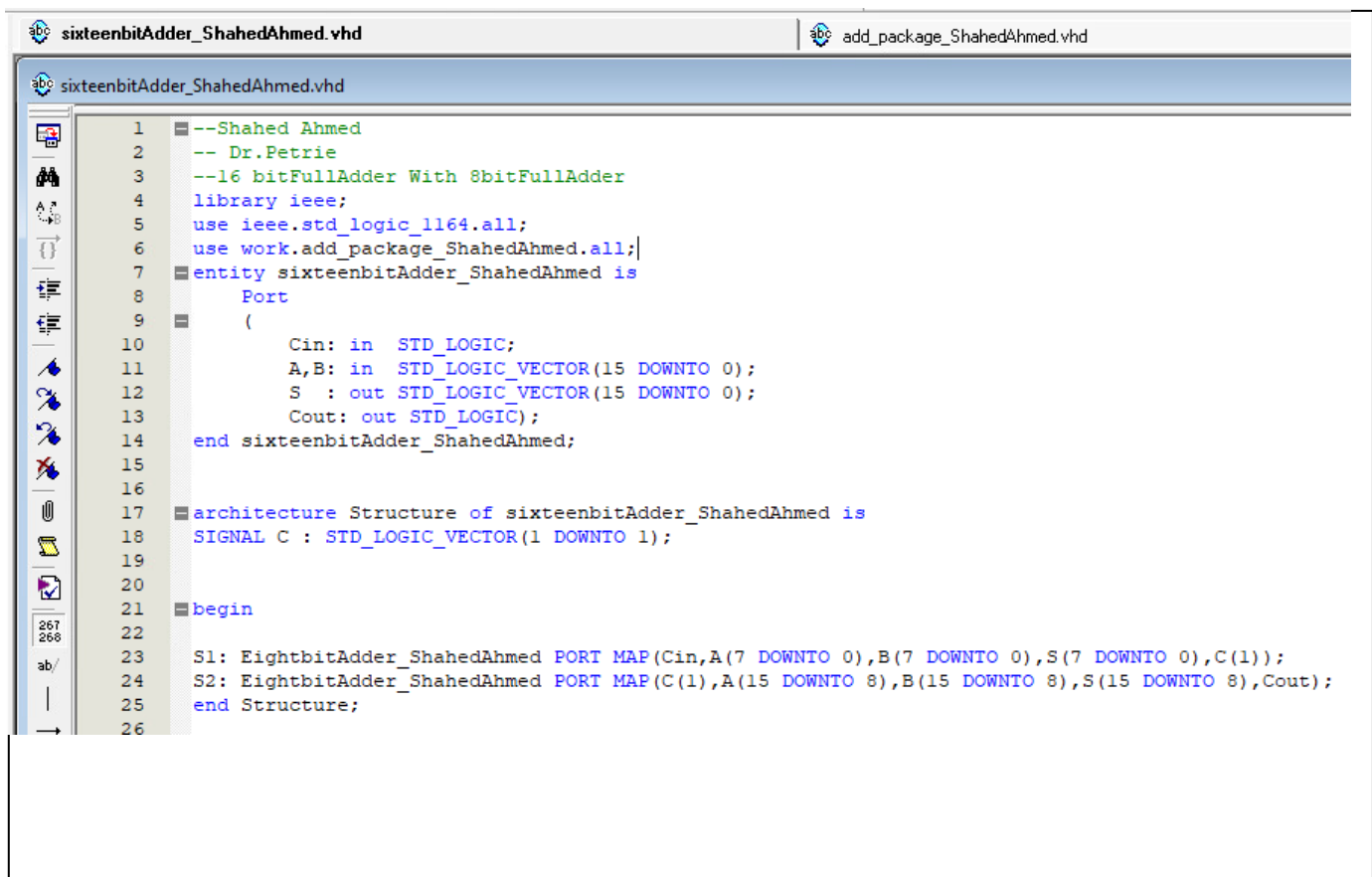

Successful Compilation

sixteenbitAdder_ShahedAhmed.vhd

add_package_ShahedAhmed.vhd

Compiler Tool

sixteenbitAdder_ShahedAhmed.vhd

```
1  --Shahed Ahmed
2  -- Dr.Petrie
3  --16 bitFullAdder With 8bitFullAdder
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use work.add_package_ShahedAhmed.all;
7  entity sixteenbitAdder_ShahedAhmed is
8      Port
9      (
10         Cin: in  STD_LOGIC;
11         A,B: in  STD_LOGIC_VECTOR(15 DOWNTO 0);
12         S   : out STD_LOGIC_VECTOR(15 DOWNTO 0);
13         Cout: out STD_LOGIC;
14     end sixteenbitAdder_ShahedAhmed;
15
16
17 architecture Structure of sixteenbitAdder_ShahedAhmed is
18     SIGNAL C : STD_LOGIC_VECTOR(1 DOWNTO 1);
19
20
21 begin
22
23     S1: EightbitAdder_ShahedAhmed PORT MAP(Cin,A(7 DOWNTO 0),B(7 DOWNTO 0),S(7 DOWNTO 0),C(1));
24     S2: EightbitAdder_ShahedAhmed PORT MAP(C(1),A(15 DOWNTO 8),B(15 DOWNTO 8),S(15 DOWNTO 8),Cout);
25 end Structure;
```

Compiler Tool

Analysis & Synthesis

100 %

00:00:06

Filter

100 %

00:00:02

Assembler

100 %

00:00:01

Classic Timing Analyzer

100 %

00:00:02

Full Compilation

100 %

00:00:11

Start

Stop


Report

Quartus II

Full Compilation was successful (5 warnings)

OK

Timing Diagram

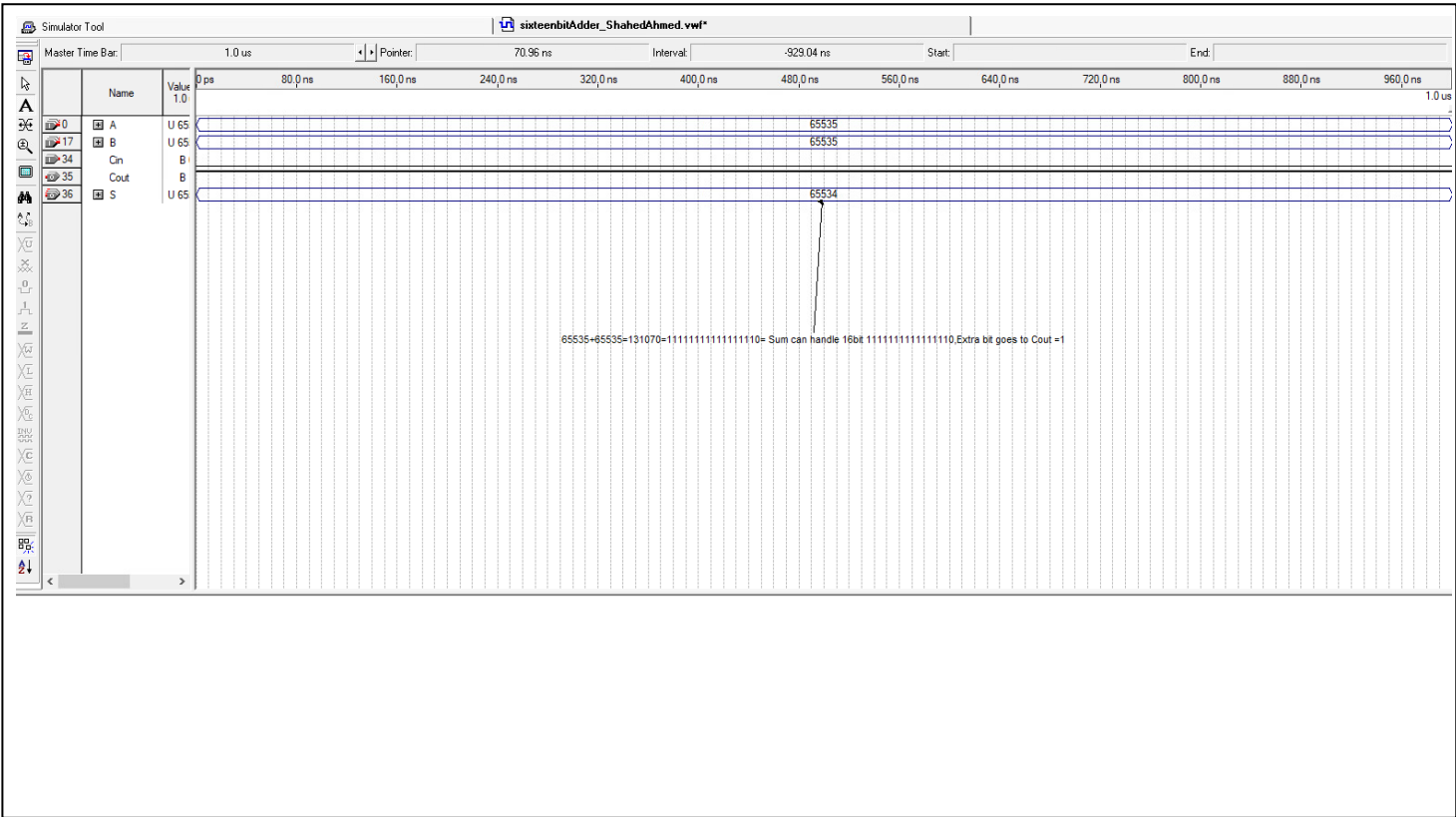

Extra Credit

Package:

```
sixteenbitAdder_ShahedAhmed.vhd | add_package_ShahedAhmed.vhd

1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;
3
4  PACKAGE add_package_ShahedAhmed IS
5  COMPONENT FullAdder_ShahedAhmed is
6  port
7  (
8      A,B,Cin : in STD_LOGIC;
9      Cout,Sum: out STD_LOGIC
10 );
11 end COMPONENT FullAdder_ShahedAhmed;
12 COMPONENT FourbitAdder_ShahedAhmed is
13
14     port
15     (
16         Cin: in  STD_LOGIC;
17         A,B: in  STD_LOGIC_VECTOR(3 DOWNTO 0);
18         S : out STD_LOGIC_VECTOR(3 DOWNTO 0);
19         Cout: out STD_LOGIC);
20 end COMPONENT FourbitAdder_ShahedAhmed;
21 COMPONENT EightbitAdder_ShahedAhmed is
22
23     Port
24     (
25         Cin: in  STD_LOGIC;
26         A,B: in  STD_LOGIC_VECTOR(7 DOWNTO 0);
27         S : out STD_LOGIC_VECTOR(7 DOWNTO 0);
28         Cout: out STD_LOGIC);
29 end COMPONENT EightbitAdder_ShahedAhmed;
30 END add_package_ShahedAhmed ;
```

NAND 3:

```
NAND3_ShahedAhmed.vhd

1  -- A library clause declares a name as a library. It
2  -- does not create the library; it simply forward declares
3  -- it.
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  entity NAND3_ShahedAhmed is
8
9      port
10     (
11         -- Input ports
12         A,B,C : in  STD_LOGIC;
13         -- Output ports
14         x      : out STD_LOGIC
15     );
16 end;
17
18 architecture Structure of NAND3_ShahedAhmed is
19
20
21 begin
22     -- fix
23     x <= (( A NAND B) NAND (A NAND B)) NAND C;
24 end;
```

NAND4:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity NAND4_ShahedAhmed is
5  port
6  (
7      -- Input ports
8      A,B,C,D : in  STD_LOGIC;
9      -- Output ports
10     x       : out STD_LOGIC
11 );
12 end;
13
14 architecture Structure of NAND4_ShahedAhmed is
15
16 begin
17
18 x <= ((A NAND B) NAND (A NAND B)) NAND ((C NAND D) NAND (C NAND D));
19
20 end;
```

display all group values in decimal: check timing diagram 4bit to 16bit

TD_LOGIC_VECTOR : Check 4 bit to 16 bit

Extra credit + if submit before Monday said by Dr.petrie